 


8/24/12

Selector


Image of a selector:



Reference: [http://www.edwardbosworth.com/My5155Text\\_V07\\_HTM/MyText5155\\_Ch06\\_V07.htm](http://www.edwardbosworth.com/My5155Text_V07_HTM/MyText5155_Ch06_V07.htm)

Barrel shifter

Image of 4 bit barrel shifter where  $C = 1$ :

 

Reference: [http://www.edwardbosworth.com/My5155Text\\_V07\\_HTM/MyText5155\\_Ch06\\_V07.htm](http://www.edwardbosworth.com/My5155Text_V07_HTM/MyText5155_Ch06_V07.htm)

4 bit barrel shifter has  $4x$  inputs and  $2s$  inputs ( $s$  inputs to specify how many bits to shift)

Example of a right cyclic shift: 101011 -> 110101

Barrel shifter is hardware logic to implement cyclic shift

Used also in computer architecture

Priority Scheduler

- First 1 in inputs from left is the only 1 value outputted
- Input: 0011 -> Output: 0010
- Useful for requests and only letting one input to access resource at a time
- If all inputs are 0 all outputs are 0

$$\begin{aligned}
 o_1 &= i_1 \\
 o_2 &= \bar{i}_1 * i_2 \\
 \dots \\
 o_k &= \bar{i}_1 * \bar{i}_2 * \dots * \bar{i}_{k-1} * i_k
 \end{aligned}$$


Area is important because of chip size. Goal is to optimize area and delay and to find the optimum tradeoff between the two.

$$\begin{aligned}
 &\bar{i}_1, \bar{i}_2, \bar{i}_3, \dots, \bar{i}_n \\
 &\{\bar{i}_1 \bar{i}_2\}, \{\bar{i}_3 \bar{i}_4\}, \{\bar{i}_5 \bar{i}_6\}, \{\bar{i}_7 \bar{i}_8\} \\
 &\{\bar{i}_1 \bar{i}_2 \bar{i}_3 \bar{i}_4\}, \{\bar{i}_5 \bar{i}_6 \bar{i}_7 \bar{i}_8\}
 \end{aligned}$$

Given these inputs n is a power of 2  
 2 in a block, need n/2 gates  
 4 in a block, need n/4 gates  
 ...  
 Area: O(n), Delay: log(n)

$$O_{12} = \bar{i}_1 * \bar{i}_2 * \bar{i}_3 * \dots * \bar{i}_{11} * i_{12}$$

At most n  
11

 

Area:  $n * \log(\log(n))$   
 Delay:  $\log(n) + \log(\log(n)) = \log(n * \log(n))$